

Sami Batuhan Basmaz Ölmez
1801042653
Computer Organization HW4
Report


Before

Instruction: 000000 00001 00010 00011 00000 100000

addn \$3, \$1, \$2

Rd = 3, Rs = 1, Rt = 2

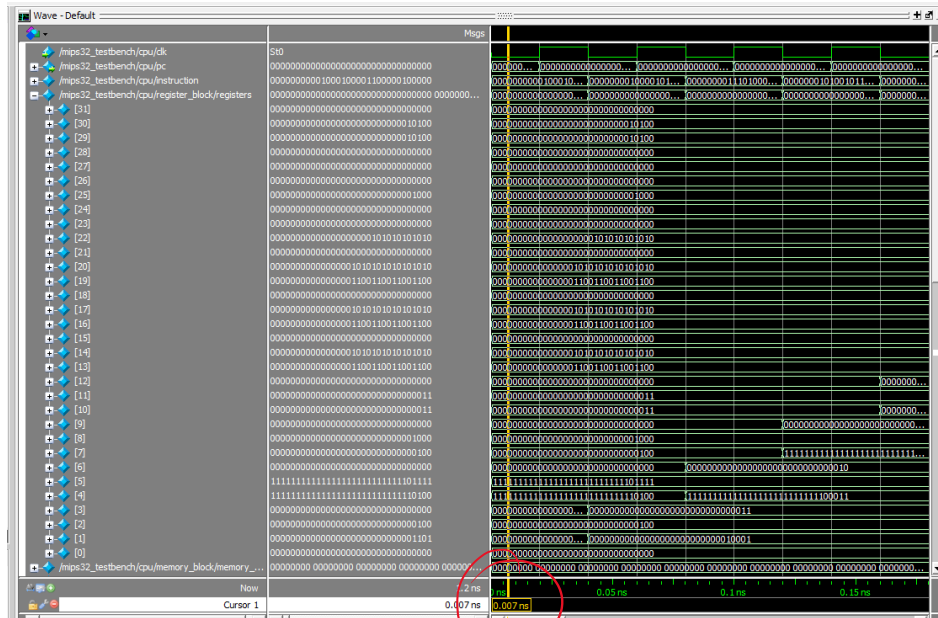Initial Decimal Values: R[3] = 0, R[1] = 13, R[2] = 4



After

Instruction: 000000 00001 00010 00011 00000 100000


addn \$3, \$1, \$2

Rd = 3, Rs = 1, Rt = 2

Expected Decimal Values: R[3] = 3, R[1] = 17, R[2] = 4

PASS!

0.040ns
Full cycle

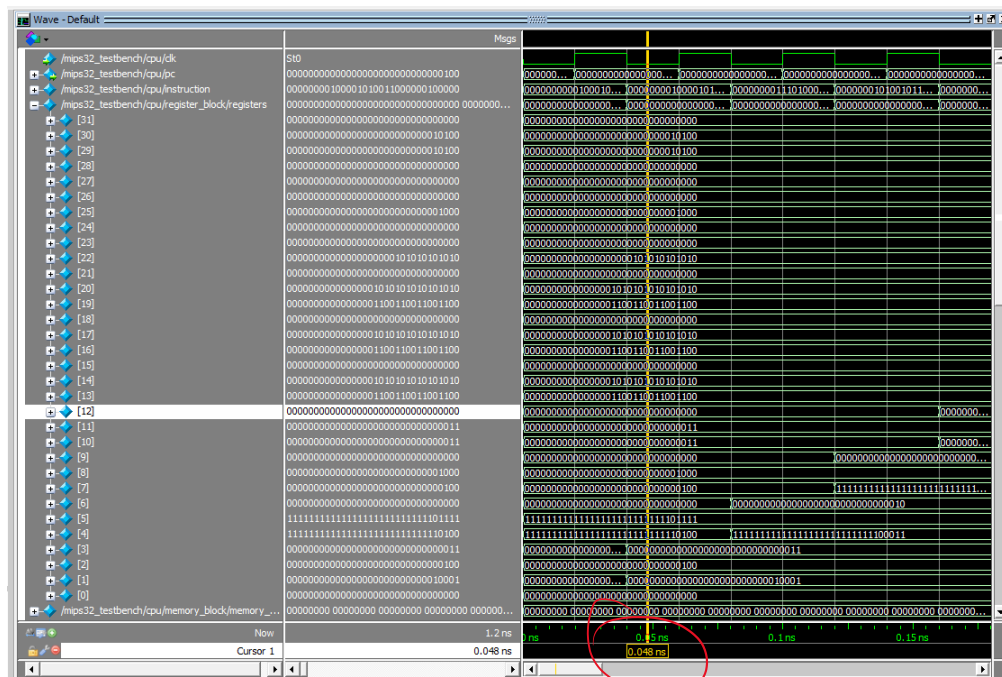


Before

Instruction: 000000 00100 00101 00110 00000 100000

addn \$6, \$4, \$5

Rd = 6, Rs = 4, Rt = 5

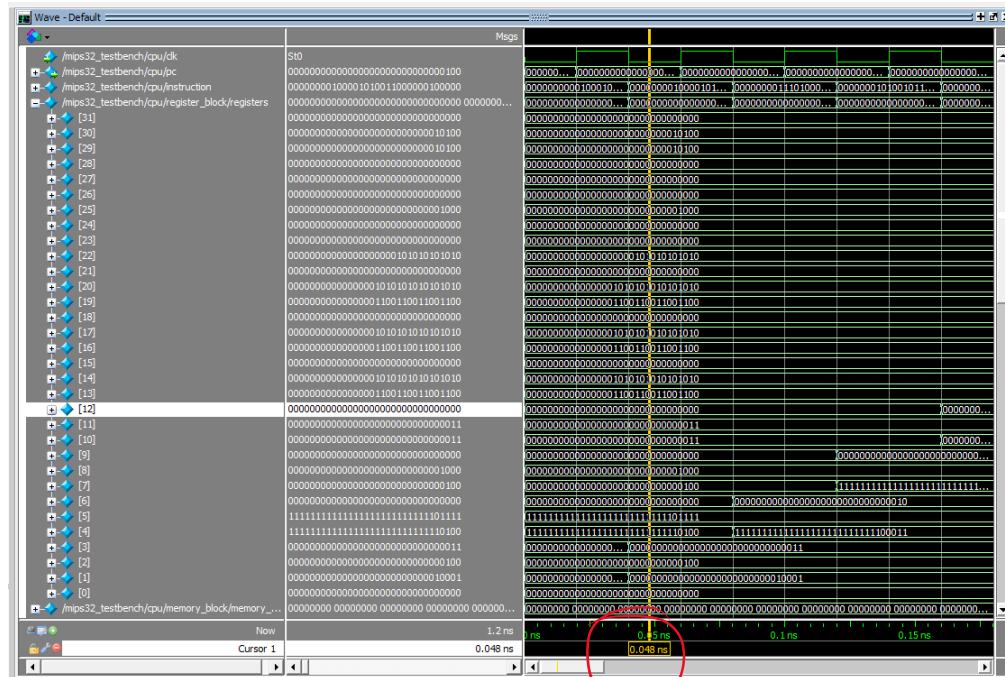Initial Decimal Values: R[6] = 0, R[4] = -12, R[5] = -17



After


Instruction: 000000 00100 00101 00110 00000 100000

addn \$6, \$4, \$5

Rd = 6, Rs = 4, Rt = 5

Expected Decimal Values: R[6] = 2, R[4] = -29, R[5] = -17

PASS!

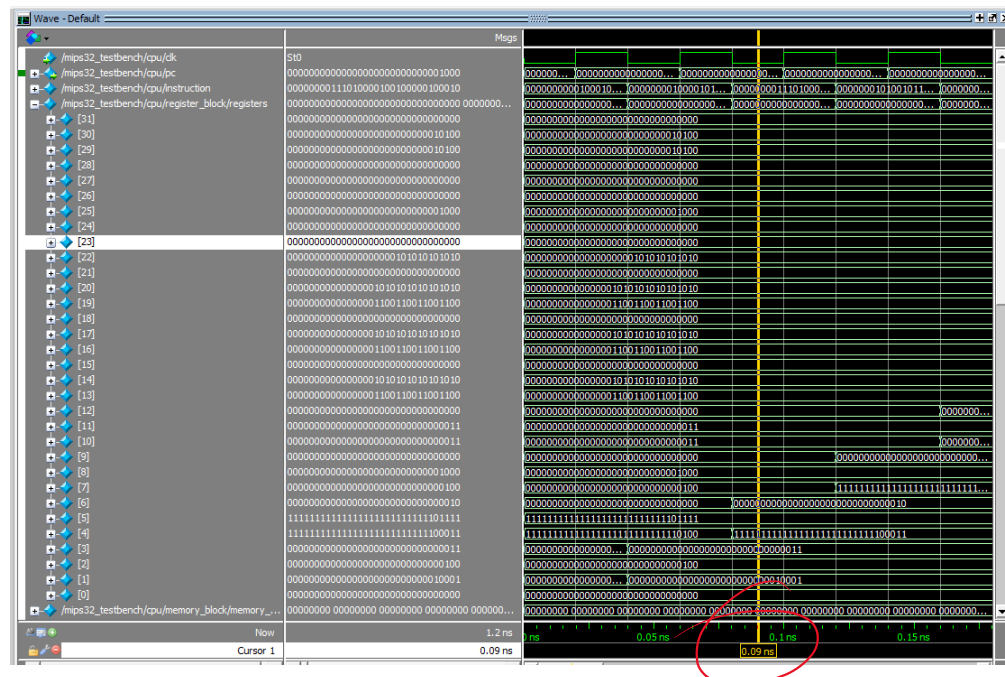


Before

Instruction: 000000 00111 01000 01001 00000 100010

subn \$9 \$7 \$8

Rd = 9, Rs = 7, Rt = 8

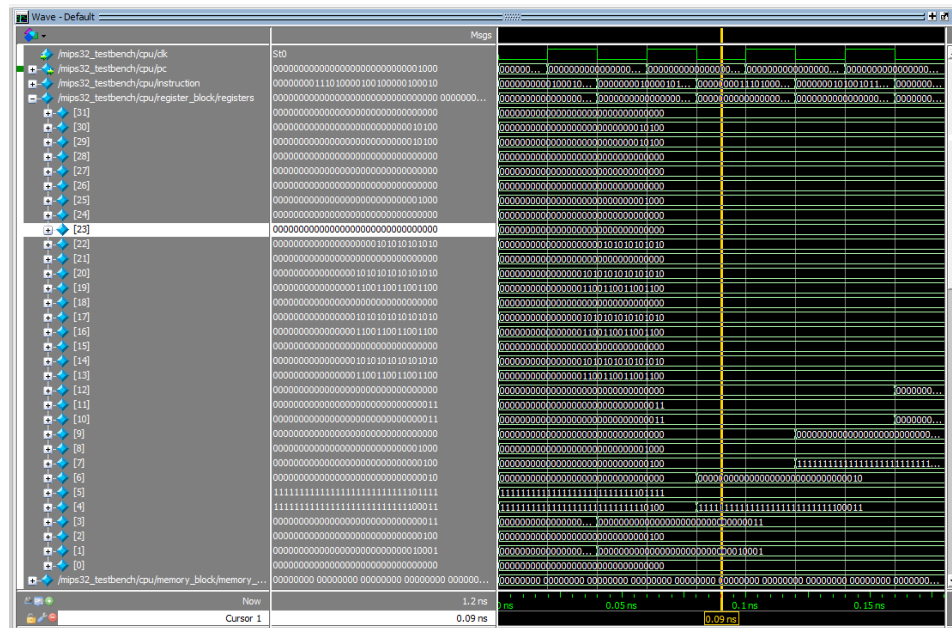Initial Decimal Values: R[9] = 0, R[7] = 4, R[8] = 8



After


Instruction: 000000 00111 01000 01001 00000 100010

subn \$9 \$7 \$8

Rd = 9, Rs = 7, Rt = 8

Expected Decimal Values: R[9] = 2, R[7] = -4, R[8] = 8

PASS!

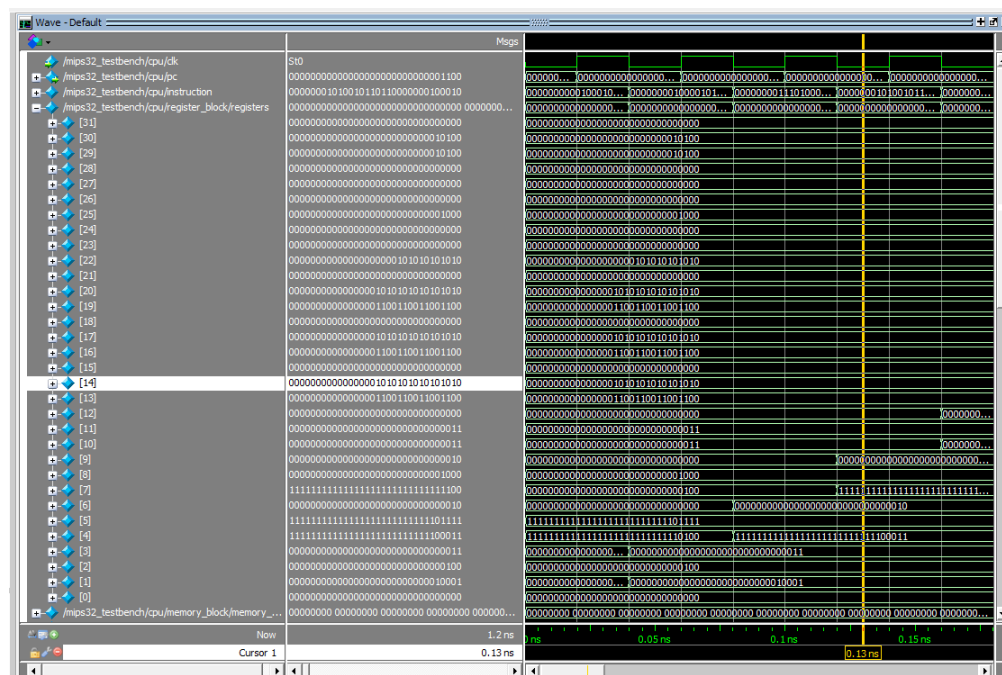


Before

Instruction: 000000 01010 01011 01100 00000 100010

subn \$12 \$10 \$11

Rd = 12, Rs = 10, Rt = 11

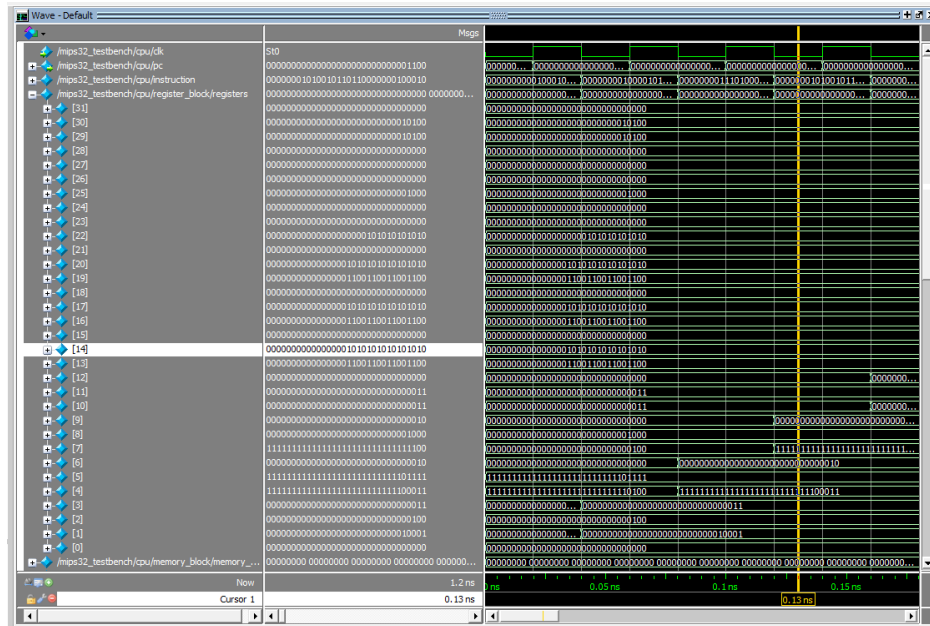Initial Decimal Values: R[12] = 0, R[10] = 3, R[11] = 3



After


Instruction: 000000 01010 01011 01100 00000 100010

subn \$12 \$10 \$11

Rd = 12, Rs = 10, Rt = 11

Expected Decimal Values: R[12] = 1, R[10] = 0, R[11] = 3

PASS!

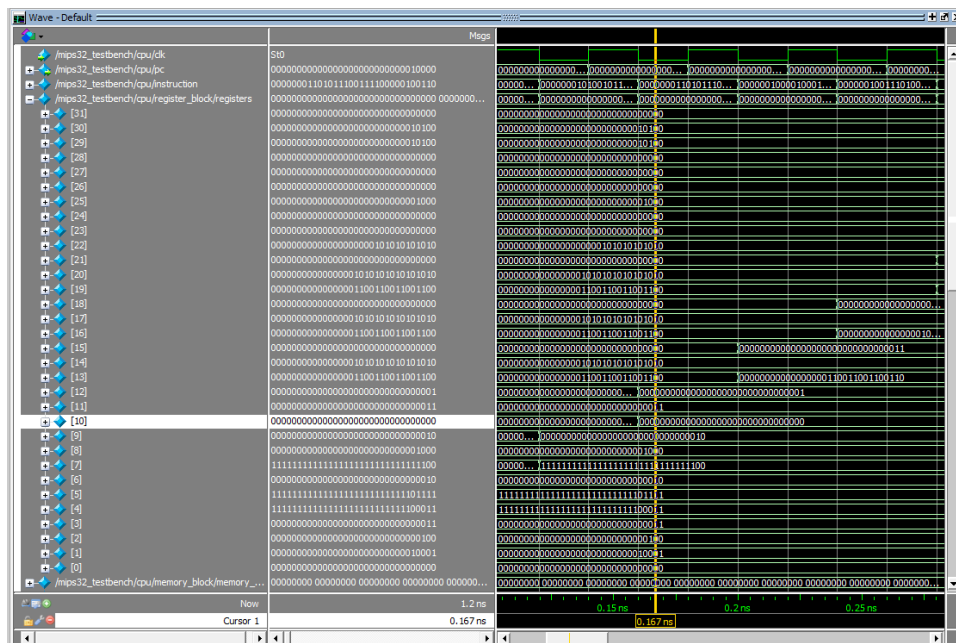

Before

Instruction: 000000 01101 01110 01111 00000 100110

xorn \$15 \$13 \$14


Rd = 15, Rs = 13, Rt = 14

Initial Binary Values:

R[15] = 32'b0,

R[13] = 000000000000000001100110011001100,

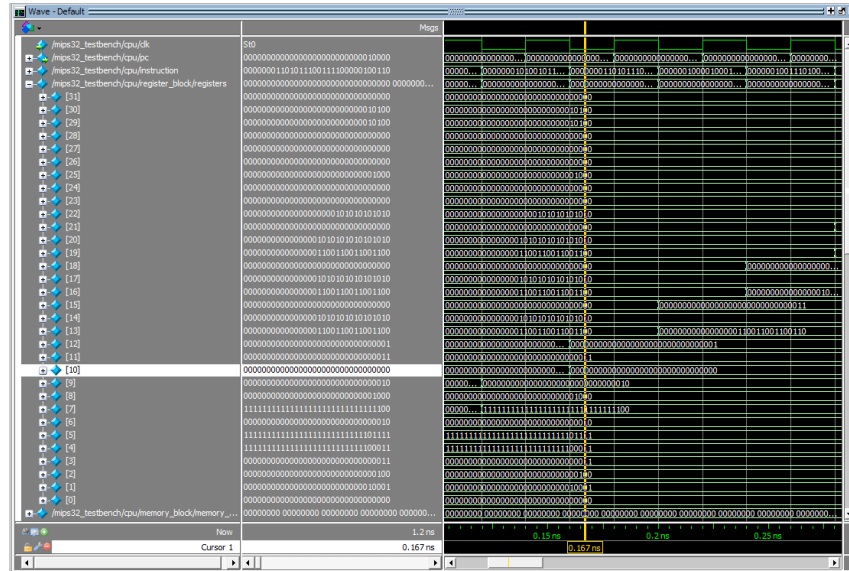R[14] = 000000000000000001010101010101010,



After

Instruction: 000000 01101 01110 01111 00000 100110

xorn \$15 \$13 \$14

Rd = 15, Rs = 13, Rt = 14


Expected Binary Values:

R[15] = 000000000000000000000000000000011,

R[13] = 000000000000000001100110011001100,

R[14] = 000000000000000001010101010101010,

PASS!

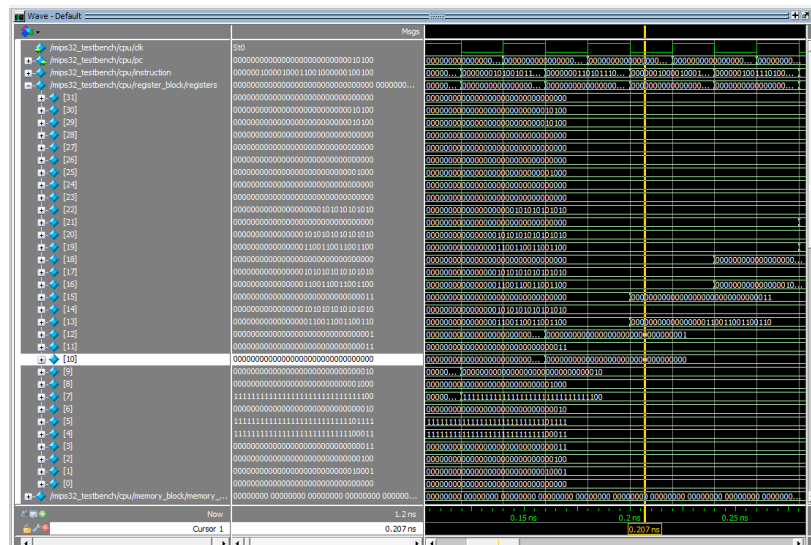

Before

Instruction: 000000 10000 10001 10010 00000 100100

andn \$18 \$16 \$17


Rd = 18, Rs = 16, Rt = 17

Initial Binary Values:

R[18] = 32'b0,

R[16] = 000000000000000001100110011001100,

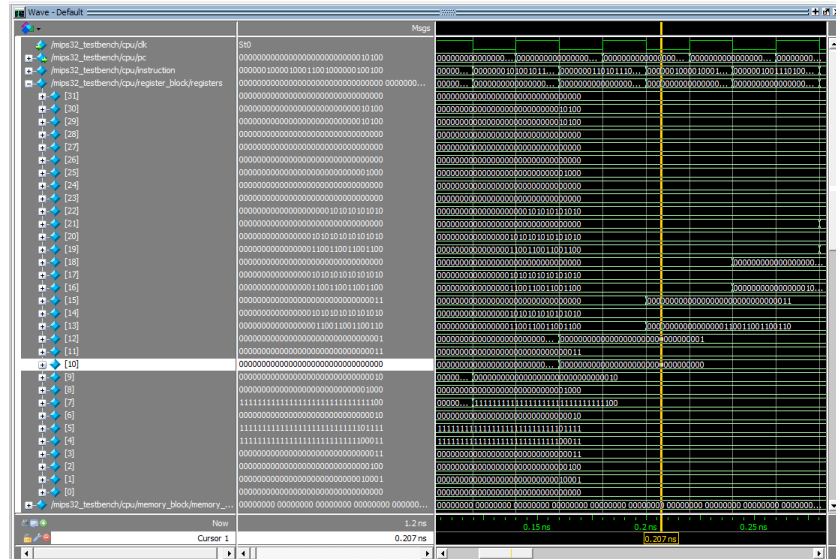R[17] = 000000000000000001010101010101010,



After

Instruction: 000000 10000 10001 10010 00000 100100

andn \$18 \$16 \$17

Rd = 18, Rs = 16, Rt = 17


Expected Binary Values:

R[18] = 000000000000000000000000000000011,

R[16] = 000000000000000001000100010001000,

R[17] = 000000000000000001010101010101010,

PASS!

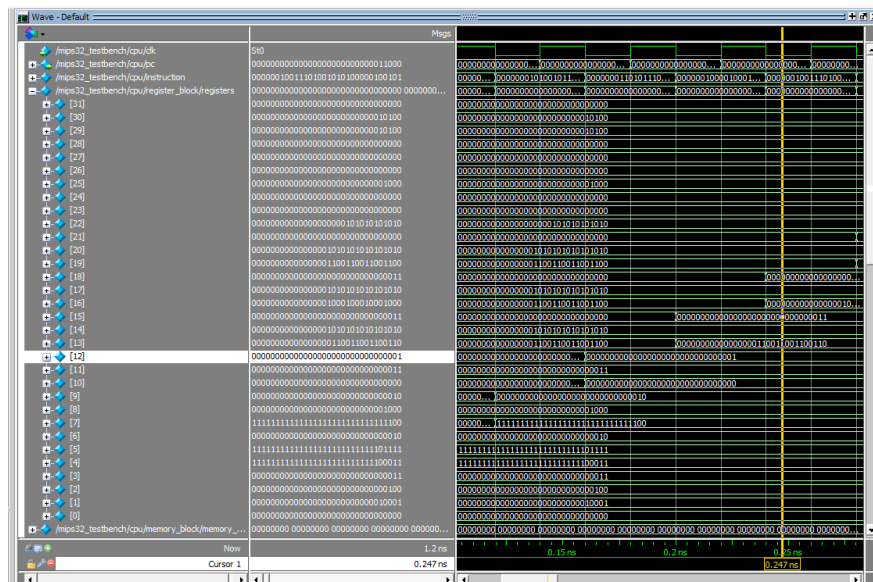

Before

Instruction: 000000 10011 10100 10101 00000 100101

orn \$21 \$19 \$20


Rd = 21, Rs = 19, Rt = 20

Initial Binary Values:

R[21] = 32'b0,

R[19] = 000000000000000001100110011001100,

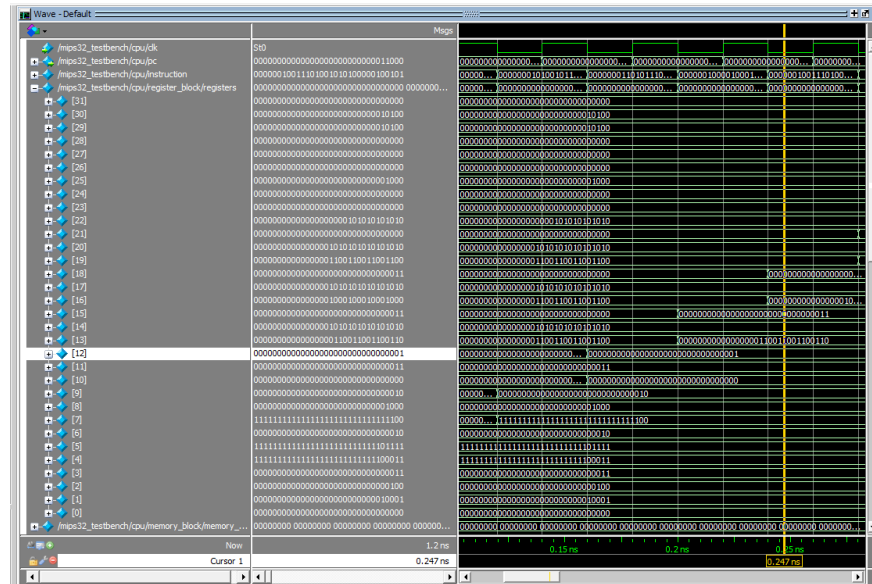R[20] = 00000000000000000101010101010101,



After

Instruction: 000000 10011 10100 10101 00000 100101

orn \$21 \$19 \$20

Rd = 21, Rs = 19, Rt = 20


Expected Binary Values:

R[21] = 00000000000000000000000000000011,

R[19] = 00000000000000000110111011101110,

R[20] = 00000000000000000101010101010101,

PASS!

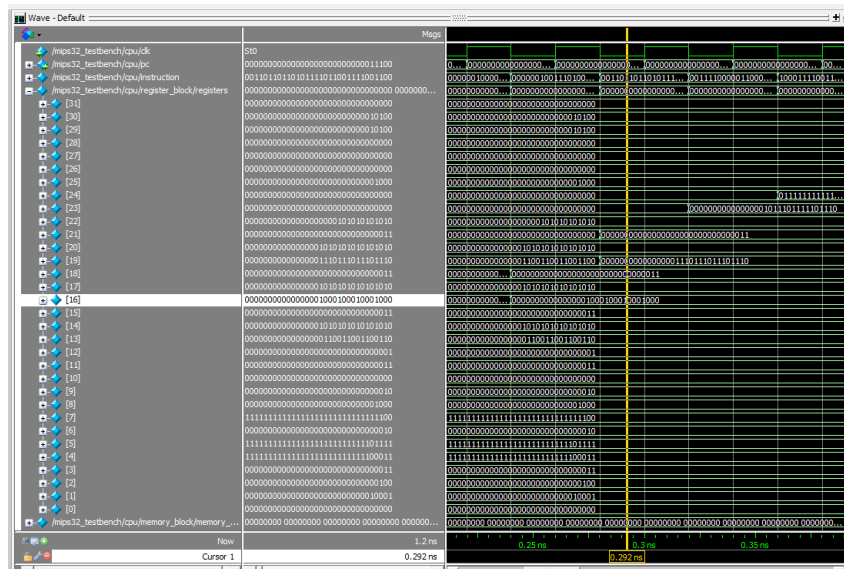

Before

Instruction: 001101 10110 10111 1011001111001100

ori \$23 \$22 1011001111001100


Rs = 22, Rt = 23

Initial Binary Values:

R[22] = 0000000000000000000000101010101010,

R[23] = 32'b0,

Immediate: 1011001111001100

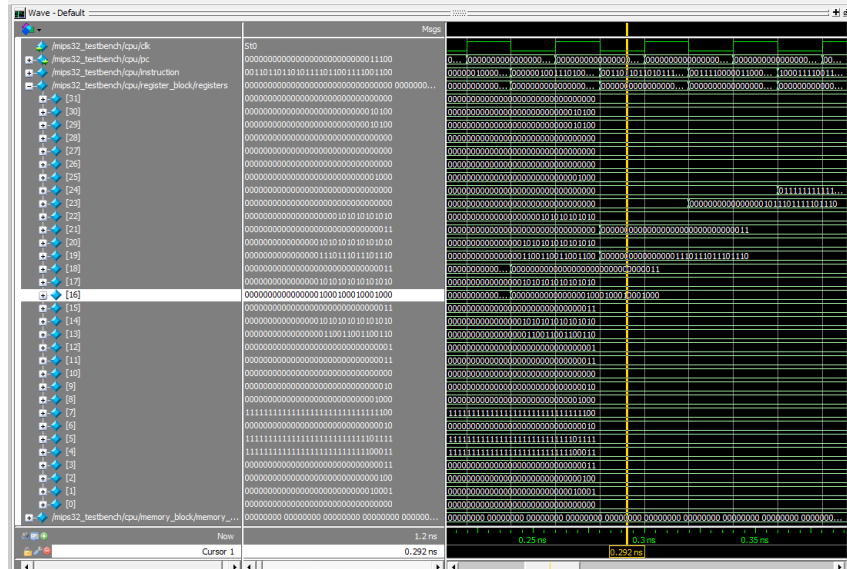

After

Instruction: 001101 10110 10111 1011001111001100

ori \$23 \$22 1011001111001100

Rs = 22, Rt = 23


Expected Binary Values:

R[22] = 00000000000000000000000101010101010,

R[23] = 00000000000000000101101111101110,

Immediate: 1011001111001100

PASS!

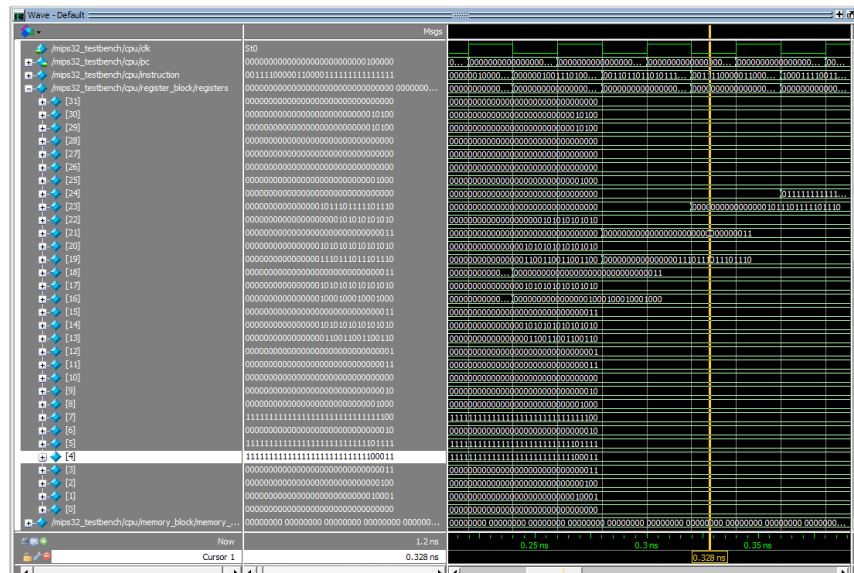

Before

Instruction: 001111 00000 11000 0111111111111111

lui \$24 0111111111111111


Rs = 0, Rt = 24

Initial Binary Values:

R[0] = 32'b0,

R[24] = 32'b0,

Immediate: 0111111111111111

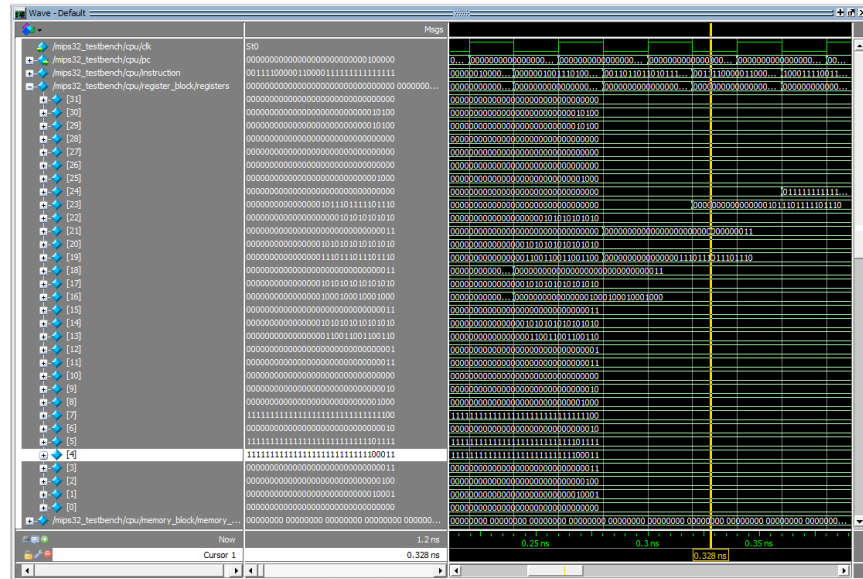

After

Instruction: 001111 00000 11000 0111111111111111

lui \$24 0111111111111111

Rs = 0, Rt = 24


Expected Binary Values:

R[0] = 32'b0,

R[24] = 01111111111111110000000000000000,

Immediate: 0111111111111111

PASS!

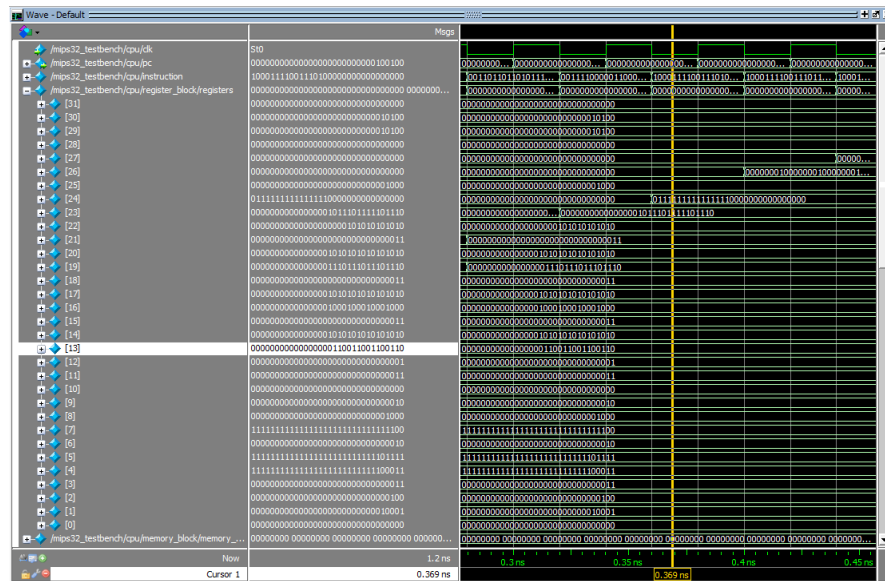

Before

Instruction: 100011 11001 11010 0000000000000000


lw \$26 0(\$25)
Rs = 25, Rt = 26

Initial Decimal Values:

R[26] = 0,

R[25] = 8,

Immediate: 0000000000000000

 

After

Instruction: 100011 11001 11010 0000000000000000

lw \$26 0(\$25)
Rs = 25, Rt = 26


Expected Binary Values:

R[26] = 00000001000000010000000100000001,

R[25] = 000000000000000000000000000001000,

Immediate: 0000000000000000

PASS!

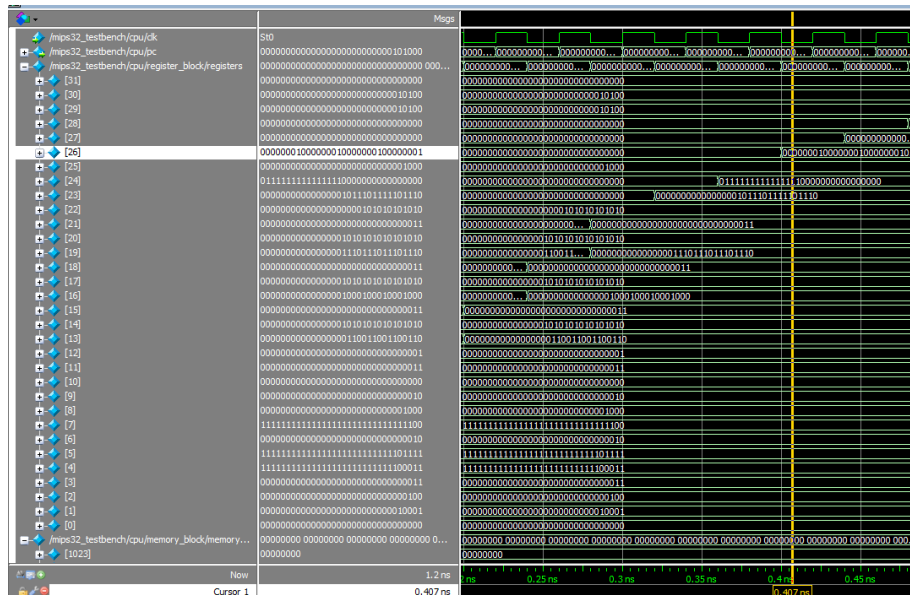

Before

Instruction: 100011 11001 11011 0000000000000100



lw \$27 4(\$25)
Rs = 25, Rt = 27

Initial Decimal Values:

R[27] = 0,

R[25] = 8,

Immediate: 0000000000000100

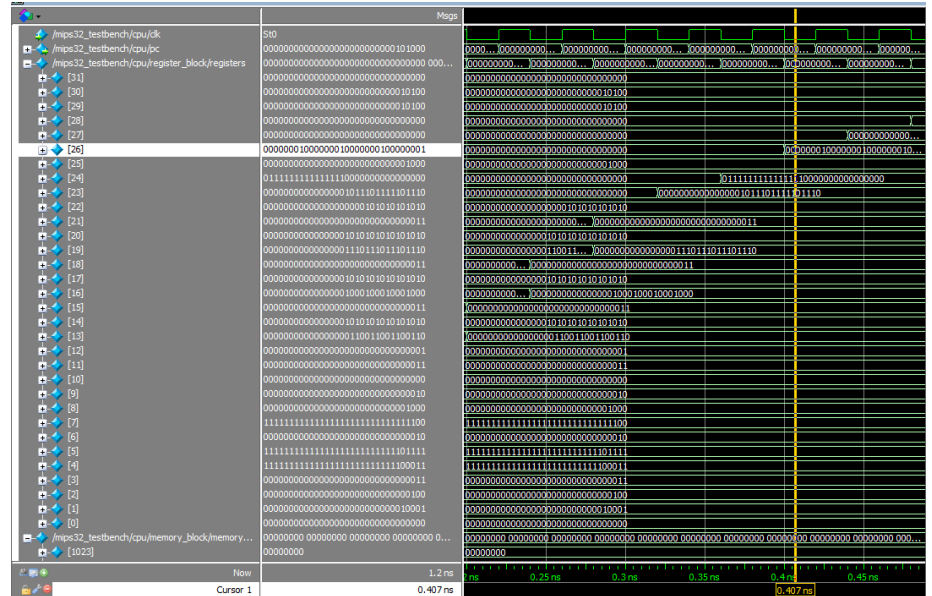 

After

Instruction: 100011 11001 11011 0000000000000100

lw \$27 4(\$25)
Rs = 25, Rt = 27


Expected Binary Values:

R[27] = 0000000000000000000000000000011110,

R[25] = 000000000000000000000000000001000,

Immediate: 0000000000000100

PASS!

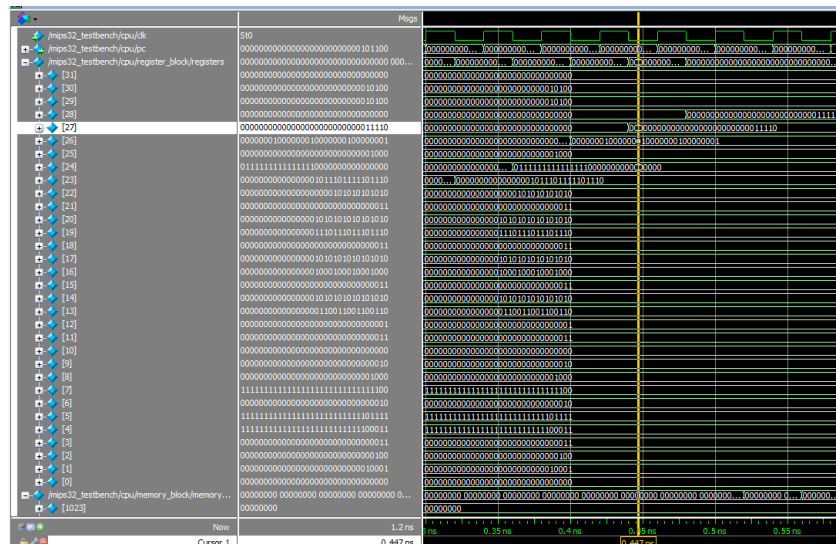

Before

Instruction: 100011 11001 11100 1111111111111100


lw \$28 -4(\$25)
Rs = 25, Rt = 28

Initial Decimal Values:

R[28] = 0,

R[25] = 8,

Immediate: 1111111111111100

 

After

Instruction: 100011 11001 11100 1111111111111100

lw \$28 -4(\$25)
Rs = 25, Rt = 28


Expected Binary Values:

R[28] = 000000000000000000000000000000001111,

R[25] = 000000000000000000000000000000001000,

Immediate: 1111111111111100

PASS!

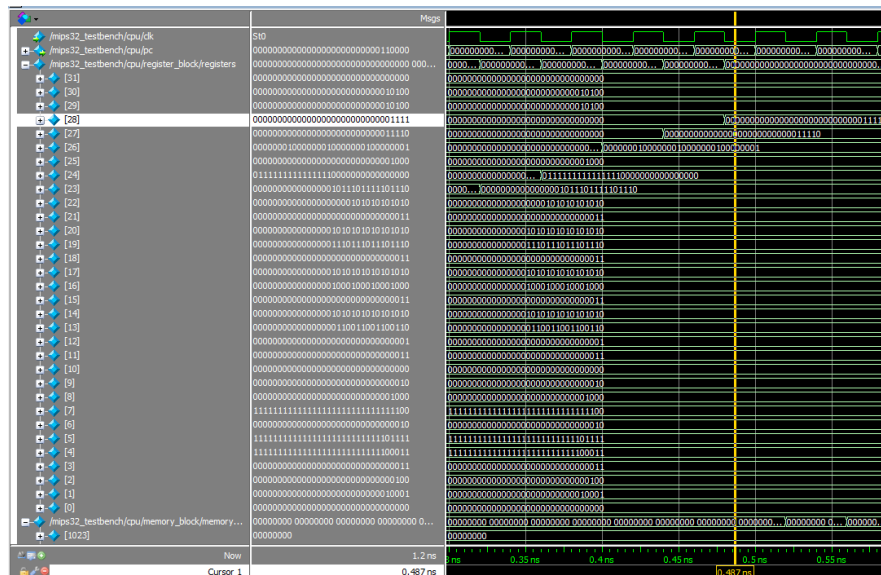

Before

Instruction: 101011 11101 11001 0000000000000000

sw \$25 0(\$29)
Rs = 29, Rt = 25


Initial Decimal Values:

M[20] = 0

R[29] = 20,

R[25] = 8,

Immediate: 0000000000000000

 

After

Instruction: 101011 11101 11001 0000000000000000

sw \$25 0(\$29)
Rs = 29, Rt = 25

Expected Decimal Values:


M[20] = 8,

R[29] = 20,

R[25] = 8,

Immediate: 0000000000000000

PASS!

 

Before

Instruction: 101011 11101 11001 000000000000100

sw \$25 4(\$29)

Rs = 29, Rt = 25


Initial Decimal Values:

M[24] = 0

R[29] = 20,

R[25] = 8,

Immediate: 0000000000000100

 

After

Instruction: 101011 11101 11001 000000000000100

sw \$25 4(\$29)

Rs = 29, Rt = 25

Expected Decimal Values:


M[24] = 8,

R[29] = 20,

R[25] = 8,

Immediate: 0000000000000100

PASS!

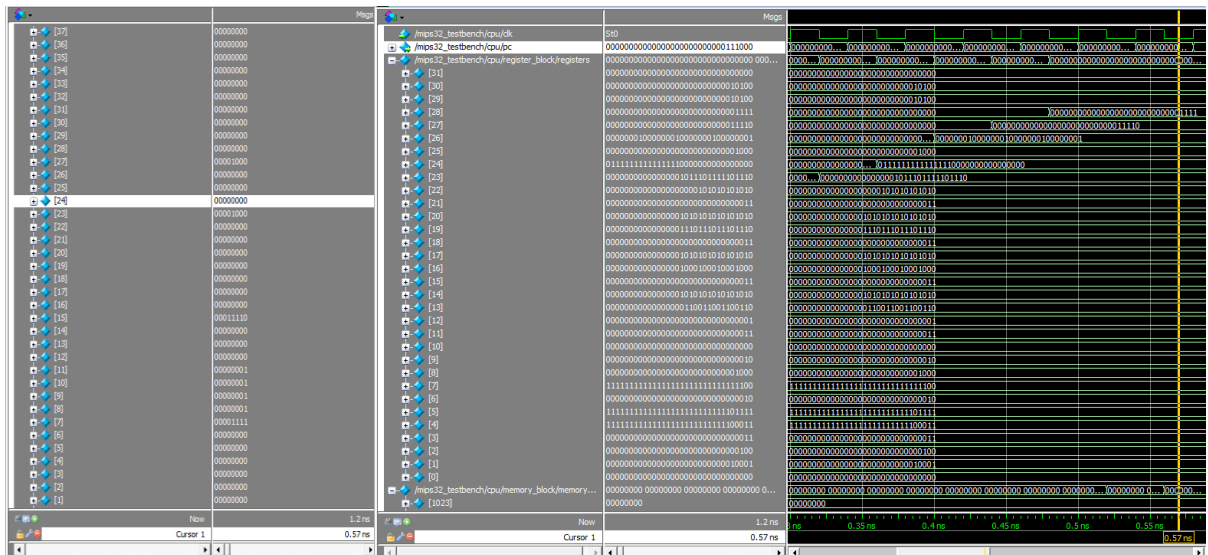

Before

Instruction: 101011 11101 11001 1111111111111100

sw \$25 -4(\$29)
Rs = 29, Rt = 25


Initial Decimal Values:

M[16] = 0

R[29] = 20,

R[25] = 8,

Immediate: 1111111111111100

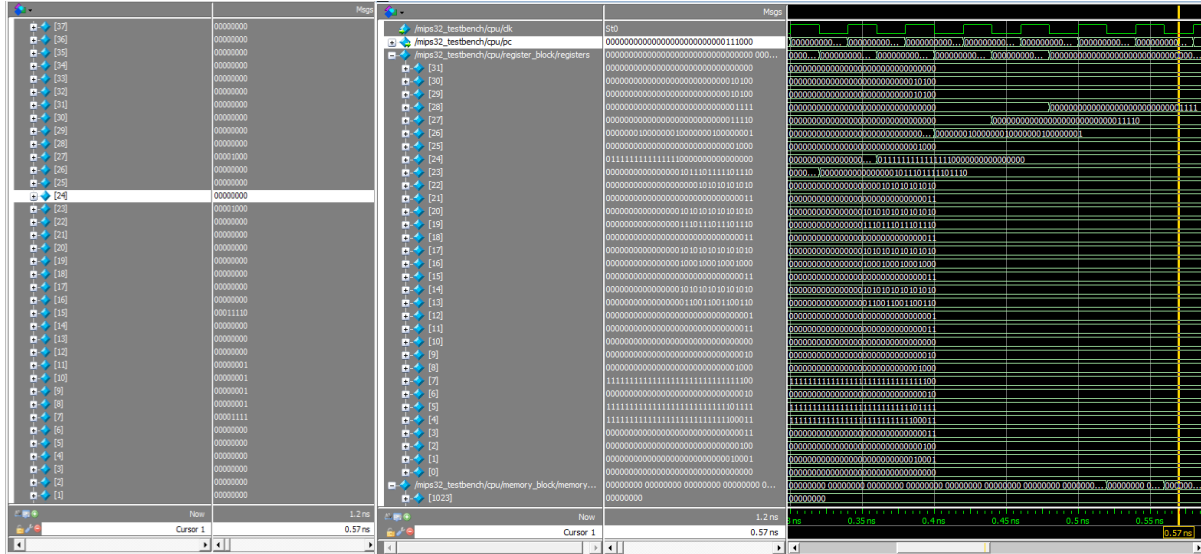

After

Instruction: 101011 11101 11001 1111111111111100

sw \$25 -4(\$29)
Rs = 29, Rt = 25

Expected Decimal Values:


M[16] = 8,

R[29] = 20,

R[25] = 8,

Immediate: 1111111111111100

PASS!

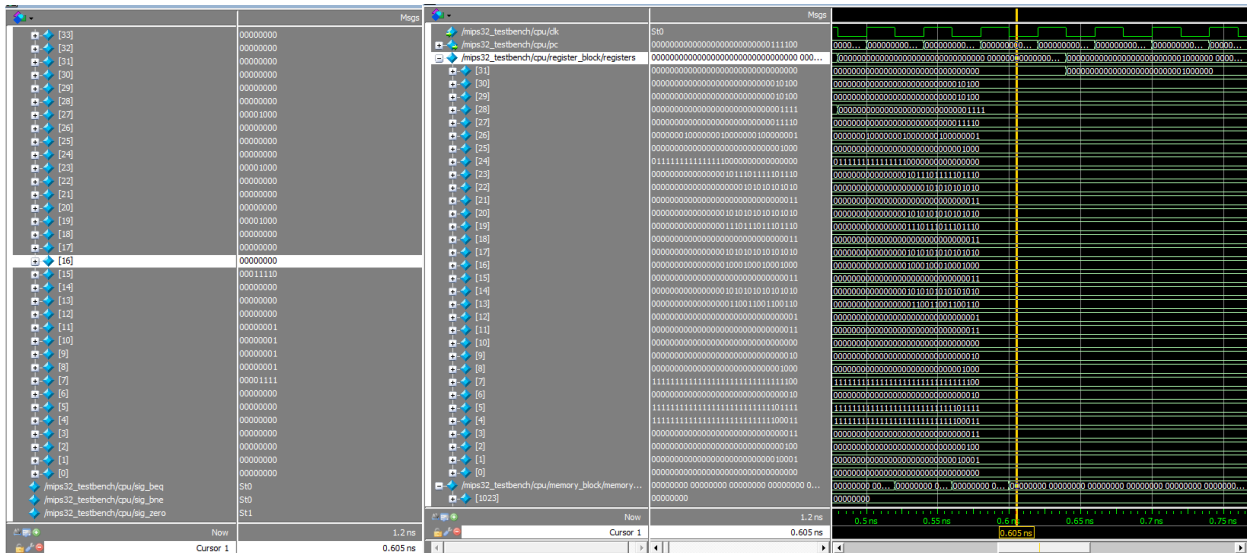

Before

Instruction: 000011 0000000000000000000010101


Jal 00000000000000000000000010101

Initial Binary Values:

R[31]=32'b0

PC=0000000000000000000000000000111100

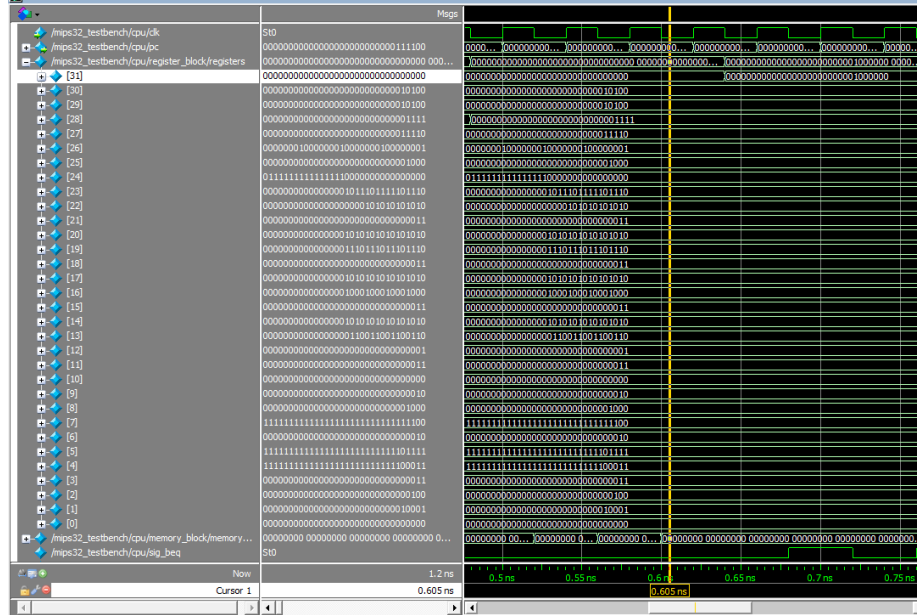Jump Addr: 00000000000000000000000000001010100



After

Instruction: 000011 00000000000000000000000010101

Jal 00000000000000000000000010101


Initial Binary Values:

R[31]=PC+4=0000000000000000000000000000100000


PC=00000000000000000000000000001010100

Jump Addr: 00000000000000000000000000001010100


PASS!

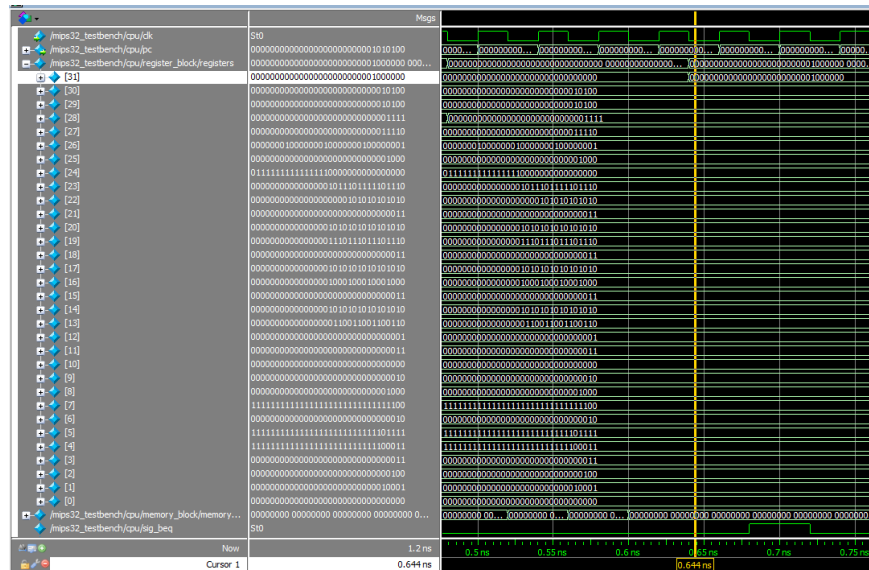

PC=000000000000000000000000001010100

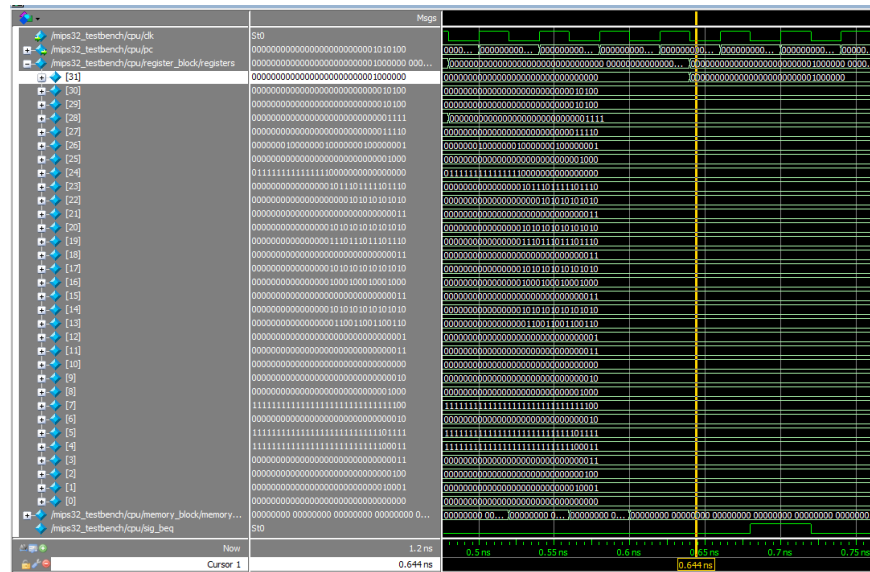[illegible]

PASS!

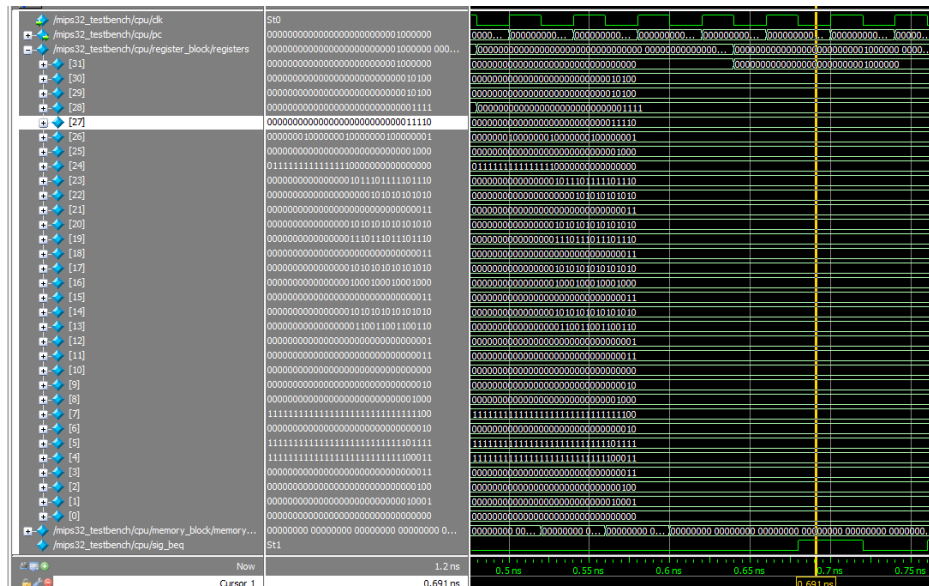

Before

Instruction: 000100 11101 11110 0000000000000011


beq \$29 \$30 3

Initial Binary Values:

R[29]=8

R[30]=8

PC=00000000000000000000000000000000

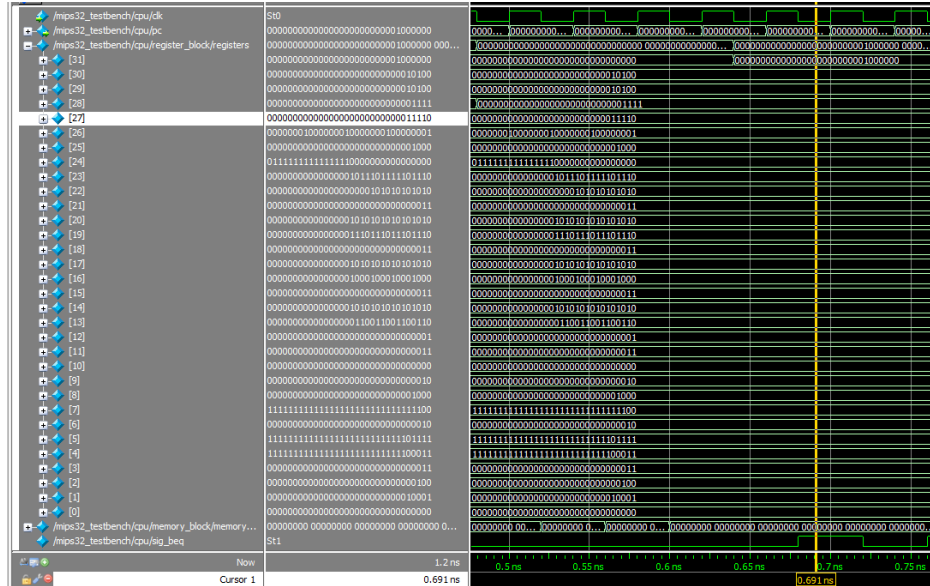

After

Instruction: 000100 11101 11110 0000000000000011

beq \$29 \$30 3, Should branch to 3 instruction after PC+4 (+16 forward in binary)


Expected Binary Values:

R[29]=8


R[30]=8

PC=0000000000000000000000000000101000

PASS!

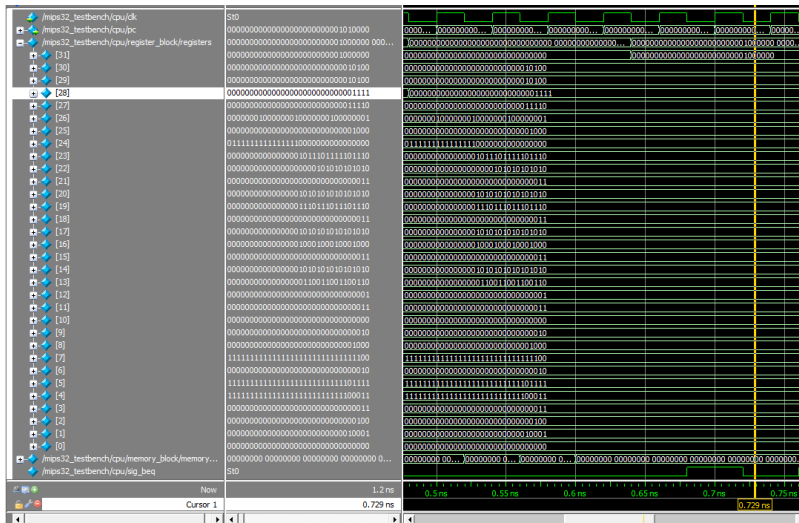

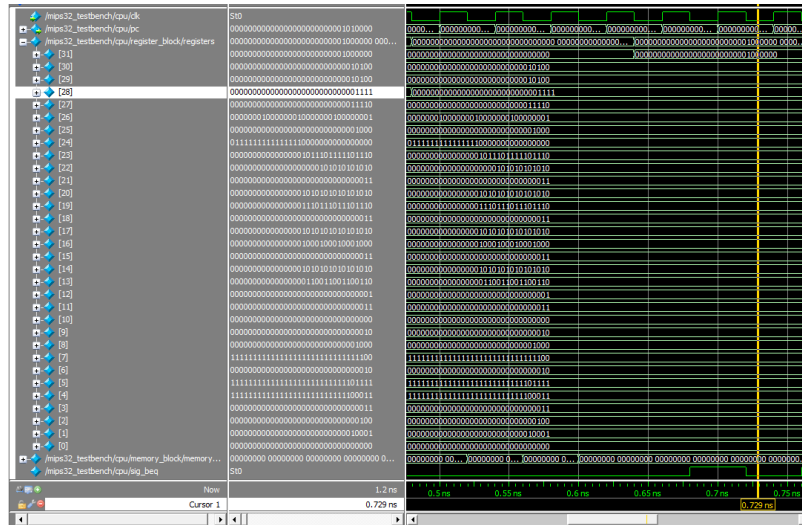
PC=000000000000000000000000000000001010000





bne \$29 \$0 -4, Should branch to 4 instruction before PC+4 (-12 backward in binary)

PC=000000000000000000000000000000001000100

PASS!

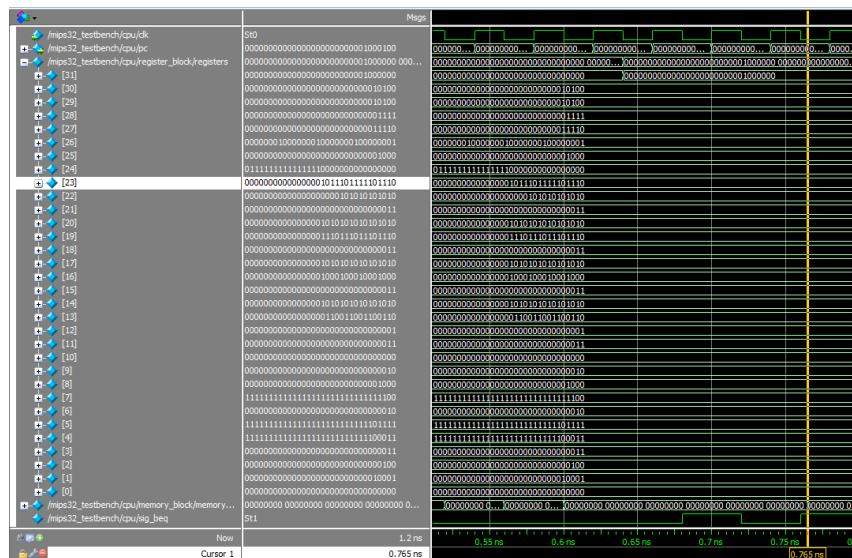

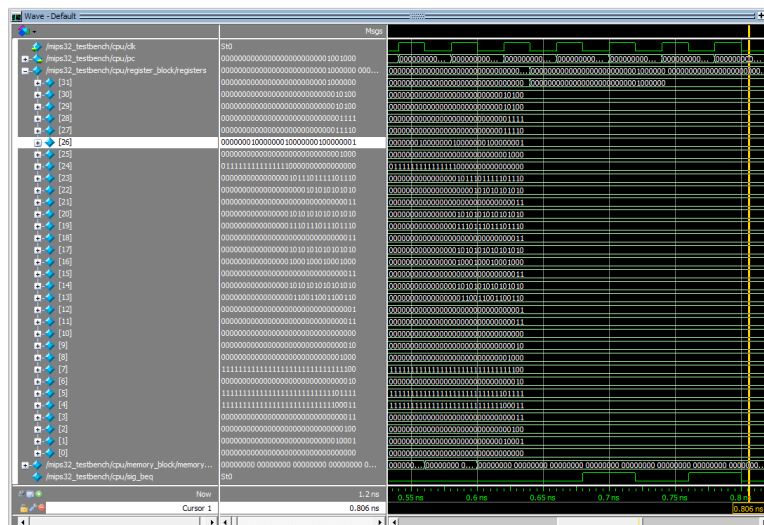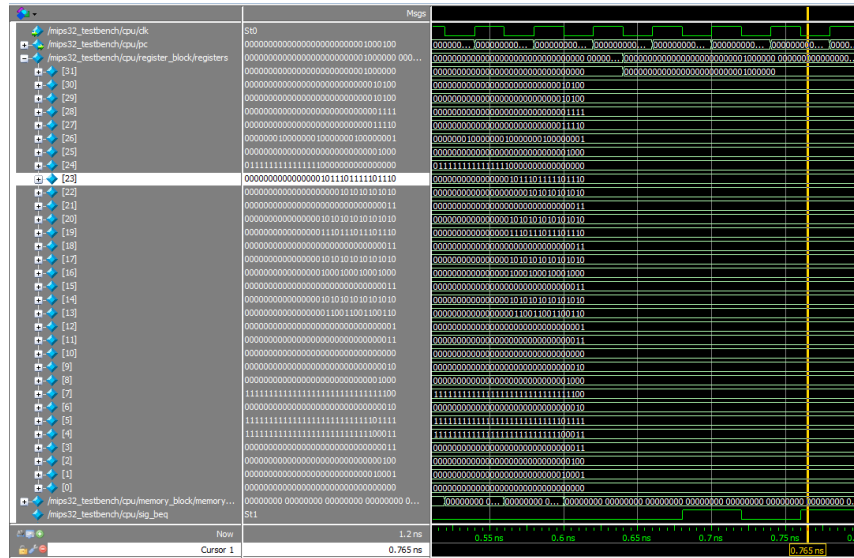


Before

Instruction: 000010 0000000000000000000010110

j 000000000000000000000000001011000

Initial

PC=000000000000000000000000001000100

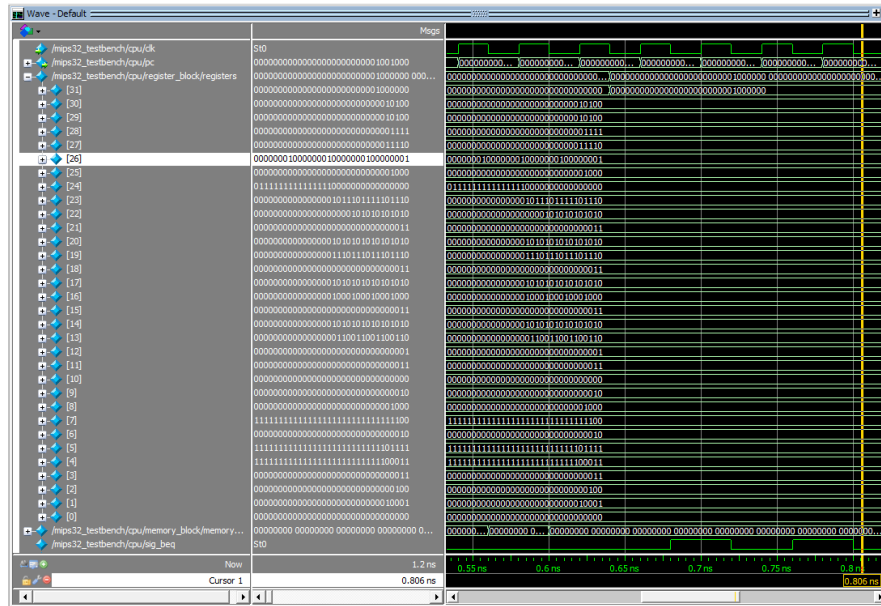

After


Instruction: 000010 00000000000000000000000010110

j 000000000000000000000000001011000

Expected

PC=000000000000000000000000001011000

PASS!

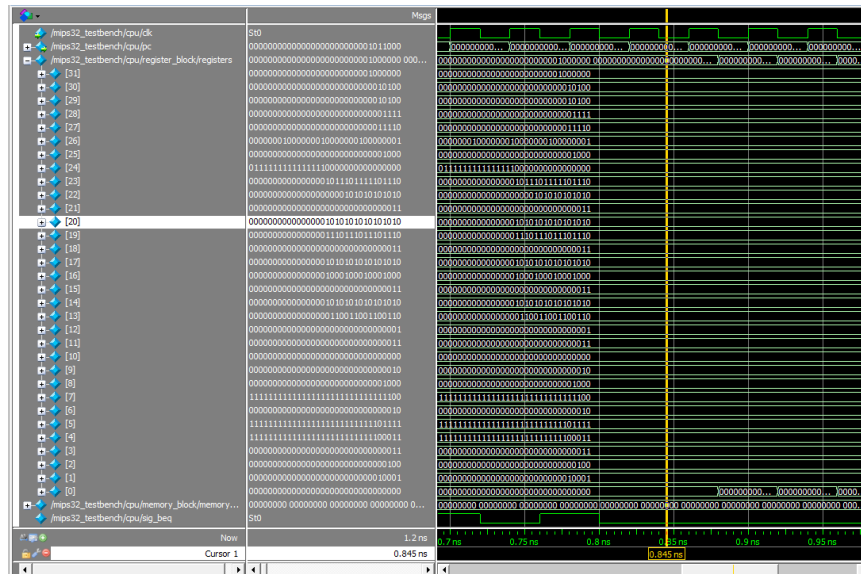

DISCLAIMER: There are 21 instruction test here. There are not 28 but these are enough for all cases. For example there are 1 test case for logics(xor,and,...) but their all edges are tested (0011, 0101). Some instructions even tested 3 times.

All In One

```
1 0000000001000100001100000100000//add $3 $1 $2
2 00000000100001010011000000100000//add $6 $4 $5
3 00000000111010000100100000100010//sub $9 $7 $8
4 000000001010010110110000000100010//sub $12 $10 $11
5 00000001101011100111100000100110//xor $15 $13 $14
6 000000010000100011001000000100100//and $18 $16 $17
7 00000010011101001010100000100101//or $21 $19 $20
8 00110110110101111011001111001100//ori $23 $22
9 00111100000110000111111111111111//lui $24
10 10001111001110100000000000000000//lw $26 $25
11 10001111001110110000000000000100//lw $27 $25
12 10001111001111001111111111111100//lw $28 $25
13 10101111011100100000000000000000//sw $25 $29
14 10101111011100100000000000000100//sw $25 $29
15 10101111011100111111111111111100//sw $25 $29
16 0000110000000000000000000010101//jal jump to jr
17 00010011101111100000000000000011//beq go 3 after pc+4 $29 == $30
18 00010011101000001111111111111100//beq fail $29 == $0
19 0000100000000000000000000010110//j jump to end
20 00000000000000000000000000000000//to show this is not worked, showing it is jumped
21 00010111101000001111111111111100//bne go back 4 after pc + 4
22 0000001111100000000000000001000//jr jump to beq $31
23 00000000000000000000000000000000
```

↳ instruction mem

```
00000000000000000000000000000000
000000000000000000000000000000001101//1==13
00000000000000000000000000000000100//2==4
000000000000000000000000000000000000//3
111111111111111111111111111110100//4==12
111111111111111111111111111101111//5==17
00000000000000000000000000000000//6
00000000000000000000000000000000100//7==4
000000000000000000000000000000001000//8==8
00000000000000000000000000000000//9
0000000000000000000000000000000011//10==3
0000000000000000000000000000000011//11==3
00000000000000000000000000000000//12
000000000000000000001100110011001100//13
0000000000000000000010101010101010//14
00000000000000000000000000000000//15
000000000000000000001100110011001100//16
0000000000000000000010101010101010//17
00000000000000000000000000000000//18
000000000000000000001100110011001100//19
0000000000000000000010101010101010//20
00000000000000000000000000000000//21
00000000000000000000101010101010//22
00000000000000000000000000000000//23
00000000000000000000000000000000//24
000000000000000000000000000000001000//25==3. mem blk
00000000000000000000000000000000//26
00000000000000000000000000000000//27
00000000000000000000000000000000//28
0000000000000000000000000000000010100//29
0000000000000000000000000000000010100//30
00000000000000000000000000000000//31

1 // memory data file (do not edit t
2 // instance=/mips32_testbench/cpu/
3 // format=bin addressradix=h datar
4 00000000000000000000000000000000
5 0000000000000000000000000000000010001
6 000000000000000000000000000000000100
7 0000000000000000000000000000000000011
8 1111111111111111111111111111100011
9 1111111111111111111111111111101111
10 00000000000000000000000000000000010
11 1111111111111111111111111111111100
12 000000000000000000000000000000001000
13 00000000000000000000000000000000010
14 00000000000000000000000000000000000
15 0000000000000000000000000000000000011
16 000000000000000000000000000000000001
17 00000000000000000000110011001100110
18 000000000000000001010101010101010
19 0000000000000000000000000000000000011
20 000000000000000001000100010001000
21 000000000000000001010101010101010
22 00000000000000000000000000000000011
23 000000000000000000001110111011101110
24 000000000000000001010101010101010
25 00000000000000000000000000000000011
26 000000000000000000000101010101010
27 00000000000000000000101110111101110
28 01111111111111111000000000000000000
29 000000000000000000000000000000001000
30 00000001000000010000000100000001
31 0000000000000000000000000000000001110
32 0000000000000000000000000000000001111
33 00000000000000000000000000000000010100
34 00000000000000000000000000000000010100
35 0000000000000000000000000000000001000000
```

↓
registers.mem


↓
registers-out-mem

1	00000000	1	// memory data file
2	00000000	2	// instance=/mips32
3	00000000	3	// format=bin address
4	00000000	4	00000000
5		5	00000000
6	00000000	6	00000000
7	00000000	7	00000000
8	00000000	8	00000000
9	00001111	9	00000000
10		10	00000000
11	00000001	11	00001111
12	00000001	12	00000001
13	00000001	13	00000001
14	00000001	14	00000001
15		15	00000001
16	00000000	16	00000000
17	00000000	17	00000000
18	00000000	18	00000000
19	00011110	19	00011110
20		20	00000000
21	00000000	21	00000000
22	00000000	22	00000000
23	00000000	23	00001000
24	00000000	24	00000000
25		25	00000000
26	00000000	26	00000000
27	00000000	27	00001000
28	00000000	28	00000000
29	00000000	29	00000000
30		30	00000000
31	00000000	31	00001000
32	00000000	32	00000000
33	00000000	33	00000000
34	00000000	34	00000000
35		35	00000000
36	00000000	36	00000000
37	00000000	37	00000000
38	00000000	38	00000000
39	00000000	39	00000000
40		40	00000000
41	00000000	41	00000000
42	00000000	42	00000000
43	00000000	43	00000000
44	00000000	44	00000000
45	00000000	45	00000000
46	00000000	46	00000000
47	00000000	47	00000000
48	00000000	48	00000000
49	00000000	49	00000000

data-mem

data-out-mem


RTL View

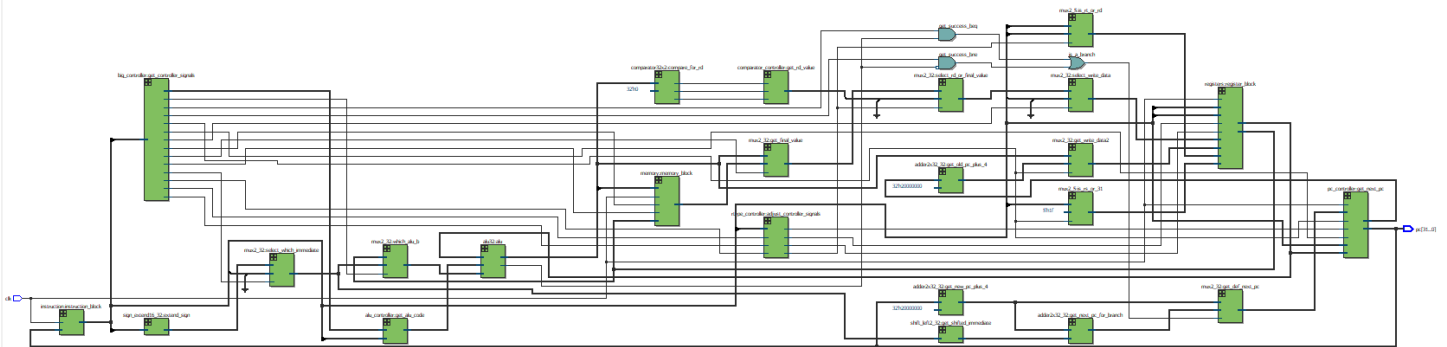

PLAYGROUND


These are my things that I did while doing this homework.

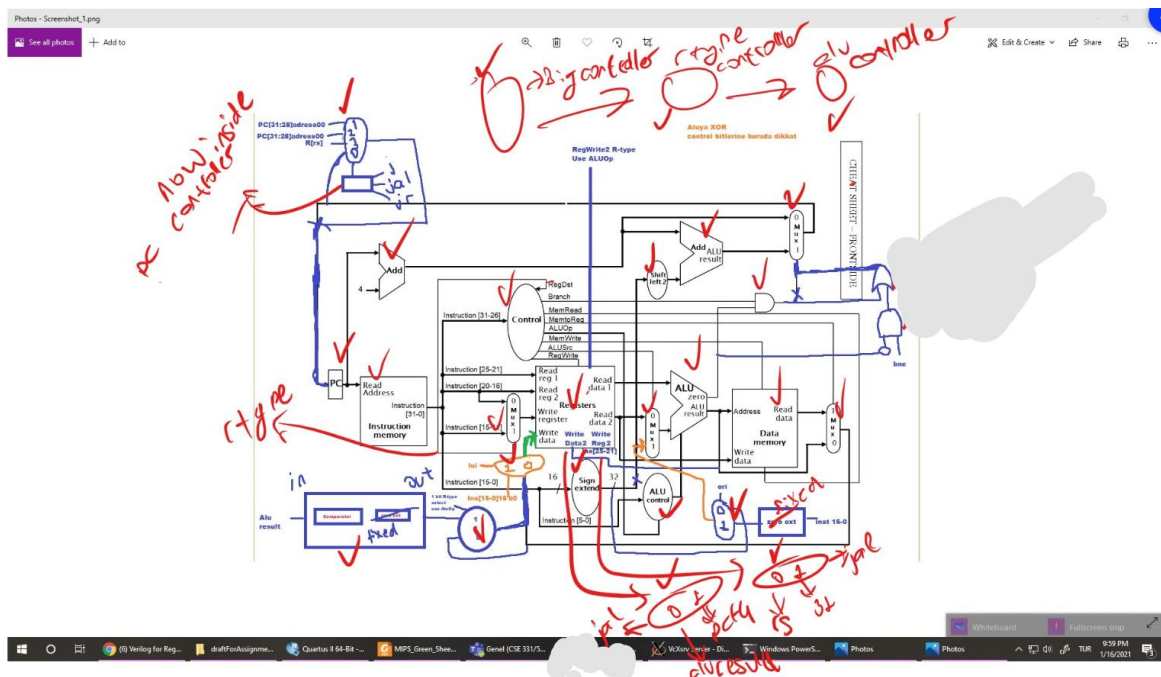DISCLAIMER: These may not represent the final form as I do changes on the fly and doesn't reflect them in these.




1-Bit ALU

 - The full adder, an xor gate, and a 4-to-1 mux are combined to form a 1-bit ALU.



ALUOp	Function
000	AND
001	OR
010	ADD
110	SUBTRACT
011	XOR

 

Comparator
two's complement
fix

$$+ = 0$$

$$- = 1$$

a _i	b _i	lt	eq	gt
+	+	1	x	x
x	x	x	1	x
+	+	x	x	1
-	+	1	x	x
-	-	1	x	x
+	-	1	x	x
-	+	x	x	1
-	-	x	x	1
+	-	x	x	1

lt	eq	gt
1	0	0
0	1	0
0	0	1
1	0	0
0	0	1
1	0	0
1	0	0
0	0	1

$$lt_0 = lt_s b' + gt_s a$$

$$gt_0 = gt_s a' + lt_s b$$

$$eq_0 = eq$$

* Big Control

	opcodes	00 0000	00 0010	00 0011	10 0011	10 1011	00 0100	00 0101	00 1101	00 1111
		R-Type	J	JAL	LW	SW	BEQ	BNE	ORI	LUI
		<C>	<C>	<C>	<C>	<C>	<C>	<C>	<C>	<C>
R-Type	RegDst/Rtype	1	0	0	0	0	0	0	0	0
LW v SW v ORI	ALUSrc	0	0	0	1	1	0	0	1	0
LW	MemToReg	0	0	0	1	0	0	0	0	0
R-Type v LW v ORI v LUI	RegWrite	1	0	0	1	0	0	0	1	1
R-Type v JAL	RegWrite2	1	0	1	0	0	0	0	0	0
LW	MemRead	0	0	0	1	0	0	0	0	0
SW	MemWrite	0	0	0	0	1	0	0	0	0
J	J	0	1	0	0	0	0	0	0	0
JAL	JAL	0	0	1	0	0	0	0	0	0
BEQ	BEQ	0	0	0	0	0	1	0	0	0
BNE	BNE	0	0	0	0	0	0	1	0	0
ORI	ORi	0	0	0	0	0	0	0	1	0
LUI	LUi	0	0	0	0	0	0	0	0	1
	ALUOp(Symbolic)	R-Type	X	X	Add	Add	Sub	Sub	OR	X
R-Type v ORI	ALUOp_{1}	1	0	0	0	0	0	0	1	0
R-Type v BEQ v BNE	ALUOp_{0}	1	0	0	0	0	1	1	0	0

* RType Controller

- Will create JR_{i} signal.
- Reforms RType because of JR being R type.

In			In	Out			Out
Function			00 1000				
RegDst/Rtype	RegWrite	RegWrite2	JR_{i}	RType	RegWrite	RegWrite2	JR_{o}
<C>	<C>	<C>	<C>	<C>	<C>	<C>	<C>
1	1	1	1	0	0	0	1
1	1	1	0	1	1	1	0
0	0	0	0	0	0	0	0
0	0	1	0	0	0	1	0
0	1	0	0	0	1	0	0
0	1	1	0	0	1	1	0

```

RType := RegDst/Rtype * !JR_{i}
JR_{o} := RegDst/Rtype * JR_{i}
RegWrite := RegWrite * !JR_{i}
RegWrite2 := RegWrite2 * !JR_{i}

```

* PC Controller

- Will take J and JAL from Big Controller, JR from ALUOp Controller.

J	JAL	JR	PCMux_{1}	PCMux_{0}
<C>	<C>	<C>	<C>	<C>
0	0	0	0	0
0	0	1	1	0
1	0	0	0	1
0	1	0	0	1

```

PCMux_{1} := !J * !JAL * JR
PCMux_{0} := J * !JAL * !JR + !J * JAL * !JR = !JR(J or JAL)

```

```

* ALU Controller

| ALUOp_{1} | ALUOp_{0} | F5_{1} | F4_{1} | F3_{1} | F2_{1} | F1_{1} | F0_{1} | OP2 | OP1 | OP0 |
|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|
| 0 | 0 | X | X | X | X | X | X | 0 | 1 | 0 |
| 0 | 1 | X | X | X | X | X | X | 1 | 1 | 0 |
| 1 | 0 | X | X | X | X | X | X | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 1 | 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 |

OP2 := !ALUOp1 * ALUOp0 + ALUOp1 * ALUOp0 * !F2 * F1 * !F0
OP1 := !ALUOp1 + ((!F2 * !F0) + (F1 * !F0))*ALUOp1*ALUOp0
OP0 := ALUOp1 * !ALUOp0 + ALUOp1*ALUOp0*F2*(F1* xor F0)

* Comparator Controller

| lt | eq | gt | o_{1} | o_{0} |
|----|----|----|----|----|
| <c> | <c> | <c> | <c> | <c> |
| 1 | 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 | 1 |

o_{1} := lt xor gt
o_{0} := eq xor gt

```

Testbenches

There are also many testbenches for other smaller parts of my design.

```

VSIM 30> step -current
# time = 0, a =0001100000000000000010001000001, b=00011000011001000010001000000001, out=00110000011001000010011001000010, expected=00110000011001000010011001000010, tresult=1
# time = 20, a =0001100000000000000000010001001101, b=000110000110010000100010000000101, out=00110000011001000010011001010010, expected=00110000011001000010011001010010, tresult=1
VSIM 31>

```

adder2x32_32

```

VSIM 39> step -current
# time = 0, a =1, b=0, ci=0, alu_code=000, ri=0, exp_ri=0, cipl=0, exp_cipl=0, tresult=1
# time = 20, a =1, b=1, ci=0, alu_code=000, ri=1, exp_ri=1, cipl=1, exp_cipl=1, tresult=1
# time = 40, a =1, b=0, ci=0, alu_code=001, ri=1, exp_ri=1, cipl=0, exp_cipl=0, tresult=1
# time = 60, a =1, b=1, ci=0, alu_code=001, ri=1, exp_ri=1, cipl=1, exp_cipl=1, tresult=1
# time = 80, a =0, b=0, ci=0, alu_code=001, ri=0, exp_ri=0, cipl=0, exp_cipl=0, tresult=1
# time = 100, a =0, b=0, ci=0, alu_code=010, ri=0, exp_ri=0, cipl=0, exp_cipl=0, tresult=1
# time = 120, a =0, b=1, ci=0, alu_code=010, ri=1, exp_ri=1, cipl=0, exp_cipl=0, tresult=1
# time = 140, a =1, b=1, ci=0, alu_code=010, ri=0, exp_ri=0, cipl=1, exp_cipl=1, tresult=1
# time = 160, a =1, b=1, ci=1, alu_code=010, ri=1, exp_ri=1, cipl=1, exp_cipl=1, tresult=1
# time = 180, a =1, b=1, ci=1, alu_code=110, ri=0, exp_ri=0, cipl=1, exp_cipl=1, tresult=1
# time = 200, a =1, b=0, ci=1, alu_code=110, ri=1, exp_ri=1, cipl=1, exp_cipl=1, tresult=1
# time = 220, a =0, b=0, ci=1, alu_code=110, ri=0, exp_ri=0, cipl=1, exp_cipl=1, tresult=1
# time = 240, a =1, b=1, ci=0, alu_code=011, ri=0, exp_ri=0, cipl=1, exp_cipl=1, tresult=1
# time = 260, a =1, b=0, ci=0, alu_code=011, ri=1, exp_ri=1, cipl=0, exp_cipl=0, tresult=1
# time = 280, a =0, b=1, ci=0, alu_code=011, ri=1, exp_ri=1, cipl=0, exp_cipl=0, tresult=1
# time = 300, a =0, b=0, ci=0, alu_code=011, ri=0, exp_ri=0, cipl=0, exp_cipl=0, tresult=1
VSIM 40>

```

Alu1


```

VSIM 59> step -current
# time = 0, a =0, b=0, lti=0, gti=0, lt=0, eq=1, gt=0, tresult=1
# time = 20, a =1, b=0, lti=0, gti=0, lt=0, eq=0, gt=1, tresult=1
# time = 40, a =0, b=1, lti=0, gti=0, lt=1, eq=0, gt=0, tresult=1
# time = 60, a =1, b=1, lti=0, gti=0, lt=0, eq=1, gt=0, tresult=1
# time = 80, a =1, b=1, lti=0, gti=1, lt=0, eq=0, gt=1, tresult=1
# time = 100, a =1, b=1, lti=1, gti=0, lt=1, eq=0, gt=0, tresult=1
# time = 120, a =1, b=0, lti=1, gti=0, lt=1, eq=0, gt=0, tresult=1

VSIM 60>

```

Comparator1x2

```

VSIM 61> step -current
# time = 0, a =00000000000000000000000000000000, b=00000000000000000000000000000000, lt=0, eq=1, gt=0, tresult=1
# time = 20, a =00000000000000000000000000000000, b=00000000000000000000000000000000, lt=0, eq=0, gt=1, tresult=1
# time = 40, a =00000000000000000000000000000000, b=00000000000000000000000000000000, lt=1, eq=0, gt=0, tresult=1
# time = 60, a =11111111111111110110000111110100, b=00000000000000000000000000000000, lt=1, eq=0, gt=0, tresult=1
# time = 80, a =00000000000000000000000000000000, b=11111111111111110011101000000000, lt=0, eq=0, gt=1, tresult=1
# time = 100, a =00000000000000000000000000000000, b=00000000000000000000000000000000, lt=0, eq=1, gt=0, tresult=1

VSIM 62>

```

Comparator32x2

```

VSIM 63> step -current
# time = 0, lt=1, eq=0, gt=0, out=10, expected=10, tresult=1
# time = 20, lt=0, eq=1, gt=0, out=01, expected=01, tresult=1
# time = 40, lt=0, eq=0, gt=1, out=11, expected=11, tresult=1

VSIM 64>

```

Comparator_controller

```

VSIM 65> step -current
# time = 0, a =011111, b=011111, out=1, expected=1, tresult=1
# time = 20, a =011111, b=001111, out=0, expected=0, tresult=1

VSIM 66>

```

Equal_6x2

```

VSIM 67> step -current
# time = 0, a =1, b=0, select=0, out=1, expected=1, tresult=1
# time = 20, a =0, b=1, select=1, out=1, expected=1, tresult=1

VSIM 68>

```

Mux2_1

```

VSIM 69> step -current
# time = 0, a =1, b=0, c=0, d=0, select=00, out=1, expected=1, tresult=1
# time = 20, a =0, b=1, c=0, d=0, select=01, out=1, expected=1, tresult=1
# time = 40, a =0, b=0, c=1, d=0, select=10, out=1, expected=1, tresult=1
# time = 60, a =0, b=0, c=0, d=1, select=11, out=1, expected=1, tresult=1

VSIM 70>

```

Mux4_1

```
VSIM 71> step -current
# time = 0, out=0, expected=0, tresult=1
# time = 20, out=1, expected=1, tresult=1
VSIM 72>
```

Or1x32_1

```
# Loading workbench_1
VSIM 73> step -current
# time = 0, a =0, b=0, c=1, out=1, expected=1, tresult=1
# time = 20, a =0, b=0, c=0, out=0, expected=0, tresult=1
VSIM 74>
```

Or1x3_1

```
VSIM 75> step -current
# time = 0, a =0, b=0, c=1, d=0, out=1, expected=1, tresult=1
# time = 20, a =0, b=0, c=0, d=0, out=0, expected=0, tresult=1
VSIM 76>
```

Or1x4_1

```
# Loading workbench_1
VSIM 78> step -current
# time = 0, rtype_i=1, rtype=0, exp_rtype=0, fnctn=1000, jr=1, exp_jr=1, tresult=1
# time = 20, rtype_i=0, rtype=0, exp_rtype=0, fnctn=1000, jr=0, exp_jr=0, tresult=1
# time = 40, rtype_i=1, rtype=1, exp_rtype=1, fnctn=101000, jr=0, exp_jr=0, tresult=1
# time = 60, rtype_i=0, rtype=0, exp_rtype=0, fnctn=101000, jr=0, exp_jr=0, tresult=1
VSIM 79>
```

Rtype_controller

```
# Loading workbench_1
VSIM 80> step -current
# time = 0, out=11010110100010001101011010001000, a=00110101101000100011010110100010
# time = 20, out=00010110100010001101011010001000, a=00000101101000100011010110100010
VSIM 81>
```

Shift_left2_32

```
VSIM 82> step -current
# time = 0, out=0000000000000000000011010110100010, a=0011010110100010
# time = 20, out=11111111111111111111011010110100010, a=1011010110100010
VSIM 83>
```

Sign_extend16_32

Warnings Explained

2020 年 12 月 12 日 星期六 09:00

Because initialized in mips32_testbench.v

13024 Output pins are stuck at VCC or GND

! 13410 Pin "pc[0]" is stuck at GND

! 13410 Pin "pc[1]" is stuck at GND

This is expected as PC consists of bytes and we start from 0 and update by multiples of 4.

DISCLAIMER: PDF specifies that there will be no input to mips32 but there should be at least one because synthesizer errors about top level has no logic. Also there should be one output too, as it gives a warning for that too.

DISCLAIMER: I put x_out.mem files in quartus project to make them appear after modelsim testbench run in quartus to make instructor's life easier. They are initially all empty!!! Output files doesn't overwrite input files!

DISCLAIMER: 256KB and 16KB memory and instruction were taking too long time to synthesize. They are easily changeable. Follow the comment instructions at the relevant places. They are currently both 1KB.